

Quiz 2 Problem 1

(a) Find the differential equation and nature response (15%)

1. The capacitor current is given by:

$$i_C(t) = C \frac{dv_{\text{out}}}{dt} = -\beta i(t).$$

2. The input voltage is expressed as:

$$v_{\text{in}}(t) = L \frac{di}{dt} + i(t) R.$$

3. Using the capacitor current relation, we have:

$$C \frac{dv_{\text{out}}}{dt} = -\beta i(t) \implies i(t) = -\frac{C}{\beta} \frac{dv_{\text{out}}}{dt}.$$

4. Substitute the expression for $i(t)$ into the equation for $v_{\text{in}}(t)$ (5%):

$$v_{\text{in}}(t) = -\frac{LC}{\beta} \frac{d^2 v_{\text{out}}}{dt^2} - \frac{RC}{\beta} \frac{dv_{\text{out}}}{dt}.$$

With the given numerical values

$$L = 1 \text{ H}, \quad R = 5 \Omega, \quad C = 0.5 \text{ F}, \quad \beta = 10,$$

this becomes:

$$v_{\text{in}}(t) = -0.05 \frac{d^2 v_{\text{out}}}{dt^2} - 0.25 \frac{dv_{\text{out}}}{dt}.$$

5. **Natural (Homogeneous) Response:** Setting $v_{\text{in}}(t) = 0$ yields

$$\frac{d^2 v_{\text{out}}}{dt^2} + 5 \frac{dv_{\text{out}}}{dt} = 0.$$

The corresponding characteristic equation

$$s(s + 5) = 0$$

has roots $s = 0$ and $s = -5$, so the general natural response is

$$v_{\text{out}}^{(n)}(t) = K_1 + K_2 e^{-5t},$$

where K_1 and K_2 are constants determined by the initial conditions.
(10%)

(b) Forced Response (15%)

For the input

$$v_{\text{in}}(t) = -(10 + 9 e^{-2t}),$$

we substitute into the differential equation derived earlier:

$$v_{\text{in}}(t) = -(10 + 9 e^{-2t}) = -\frac{LC}{\beta} \frac{d^2 v_{\text{out}}}{dt^2} - \frac{RC}{\beta} \frac{dv_{\text{out}}}{dt}$$

Since

$$v_{\text{in}}(t) = -(10 + 9 e^{-2t}),$$

we look for a particular solution of the form (5%)

$$v_{\text{out}}^{(f)}(t) = A t + B e^{-2t}.$$

Deriving the Particular Solution

- Compute the first derivative:

$$\frac{d}{dt} v_{\text{out}}^{(f)}(t) = A - 2B e^{-2t}.$$

- Compute the second derivative:

$$\frac{d^2}{dt^2} v_{\text{out}}^{(f)}(t) = 4B e^{-2t}.$$

- Substitute these into the differential equation, we have (5% each):

$$A = 40, B = -30$$

Thus, the forced response is:

$$v_{\text{out}}^{(f)}(t) = 40 t + -30 e^{-2t}.$$

2. (30%) Consider the circuit shown in Fig.


2. At $t = 0$, the switch is opened

(disconnected).

(a) (10%) Find $v_o(0^+)$.


(b) (5%) Find $v_o(\infty)$.

(c) (15%) Find $v_o(t)$.

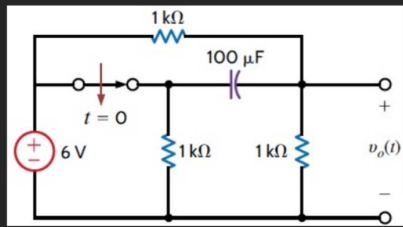

(Fig. 2)

(b)

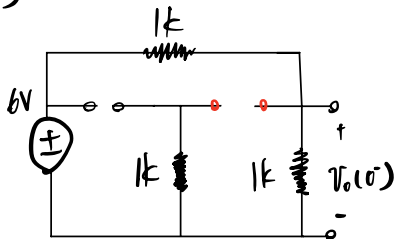


$$v_o(\infty) = 3V$$

配分 (b)

(1) 画电路 3分, 解出 $v_o(\infty)$ 2分

(2) 直接解出 $v_o(\infty)$ 3分 有结论形式

(c)

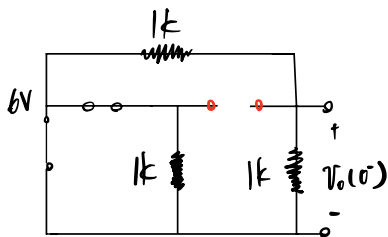

$$R_{eq} = (1k \parallel 1k) + 1k = 1.5k$$

$$\tau = RC = 1.5k \times 100\mu = 0.15$$

$$v_o(\infty) + (v_o(0^+) - v_o(\infty))e^{-t/\tau} \Rightarrow v_o(t) = 3 - 2e^{-t/0.15} V$$

配分 (c)


(1) 解出 R_{eq} 4分

(2) 解出 τ 4分

(3) 画出电路 2分, 解出 $v_o(t)$ 3分

(4) 直接解出 $v_o(t)$ 15分 有结论形式

(a) $t = 0^-$

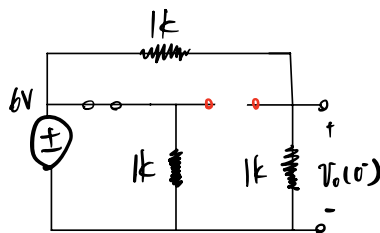

$$v_o(0^-) = 3V$$

$$v_o(0^+) = 3V$$


配分 (a)

(1) 画出 $v_o(0^-)$ 电路 4分

(2) 解出 $v_o(0^-)$ 6分

(3) 直接解出 $v_o(0^+)$ 10分 有结论形式

$t = 0^+$

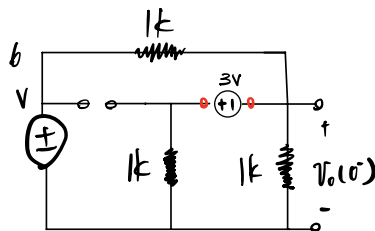

$$\frac{V_1 - 6}{1k} + \frac{V_1 + 3}{1k} + \frac{V_1}{1k} = 0$$

$$\Rightarrow V_1 = 1V$$

$$\Rightarrow v_o(0^+) = 1V$$

3.

$$(a) \quad (3) \quad i_R(t) = \frac{v_s(t) - v_C(t)}{R} \quad \text{or} \quad v_C(t) = v_s(t) - Ri_R(t)$$

$$(3) \quad i_R(t) = i_L(t) + i_C(t) \quad \text{or} \quad \frac{di_R(t)}{dt} = \frac{di_L(t)}{dt} + \frac{di_C(t)}{dt}$$

$$(3) \quad v_L(t) = L \frac{di_L(t)}{dt} \quad \text{or} \quad \frac{di_L(t)}{dt} = \frac{v_L(t)}{L}$$

$$(3) \quad i_C(t) = C \frac{dv_C(t)}{dt} \quad \text{or} \quad \frac{di_C(t)}{dt} = \frac{d^2v_C(t)}{dt^2}$$

$$\frac{di_R(t)}{dt} = \frac{v_L(t)}{L} + C \frac{d^2v_C(t)}{dt^2}$$

$$\frac{dv_C(t)}{dt} = \frac{d}{dt} [v_s(t) - Ri_R(t)]$$

$$\frac{d^2v_C(t)}{dt^2} = \frac{d^2v_s(t)}{dt^2} - R \frac{d^2i_R(t)}{dt^2}$$

$$\frac{di_R(t)}{dt} = \frac{v_s(t) - Ri_R(t)}{L} + C \left[\frac{d^2v_s(t)}{dt^2} - R \frac{d^2i_R(t)}{dt^2} \right]$$

$$(3) \quad RC \frac{d^2i_R(t)}{dt^2} + \frac{di_R(t)}{dt} + \frac{R}{L} i_R(t) = \frac{1}{L} v_s(t) + C \frac{d^2v_s(t)}{dt^2}$$

$$(b) \quad RC \frac{d^2i_R(t)}{dt^2} + \frac{di_R(t)}{dt} + \frac{R}{L} i_R(t) = \frac{1}{L} v_s(t) + C \frac{d^2v_s(t)}{dt^2}$$

$$(10) \quad t = 0^+ \quad \left\{ \begin{array}{l} i_L(0^+) = i_L(0^-) = -2(A) \\ v_C(0^+) = v_C(0^-) = 0(V) \\ i_R(0^+) = \frac{v_s(0^+) - v_C(0^+)}{R} = 6(A) \\ i_C(0^+) = i_R(0^+) - i_L(0^+) = 8(A) \\ \frac{d^2i_R(t)}{dt^2} + 10 \frac{di_R(t)}{dt} + 25i_R(t) = 150(A) \end{array} \right.$$

Homogeneous solution

$$\frac{d^2 i_R(t)}{dt^2} + 10 \frac{di_R(t)}{dt} + 25 i_R(t) = 0$$

$$r^2 + 10r + 25 = 0 \rightarrow r = -5(\text{double root})$$

$$(5) \ i_{R,h}(t) = (A + Bt)e^{-5t}$$

Particular solution

$$(5) \ 0 + 0 + 25i_{R,p}(t) = 150 \rightarrow i_{R,p}(t) = 6$$

General solution

$$i_R(0) = A + 6 = 6 \rightarrow A = 0$$

$$\frac{di_R(0)}{dt} = B = -10i_C(0) = -80$$

$$(5) \ i_R(t) = -80te^{-5t} + 6 \ (\text{when } t > 0)$$